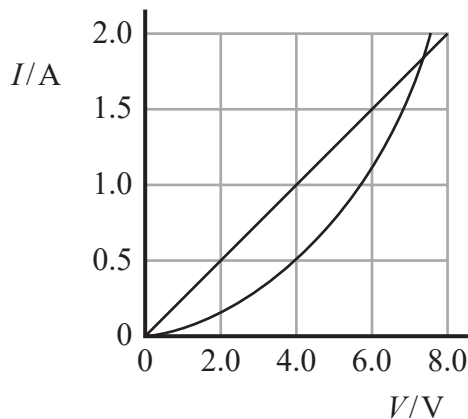


10 The current-potential difference graphs for a resistor and a thermistor are shown.



The resistor and thermistor are connected in series to a 6 V battery.

What is the current, in amps, in the resistor?

- ☐ A 0.5
- ☐ B 1.0
- ☐ C 1.5
- ☐ D 2.0

(Total for Question 10 = 1 mark)