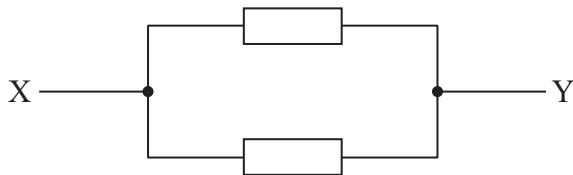


3 The two resistors shown each have resistance  $R$ .



Which expression gives the correct resistance between point X and point Y?

☐ A  $\frac{R}{2}$

☐ B  $R$

☐ C  $2R$

☐ D  $R^2$

(Total for Question 3 = 1 mark)