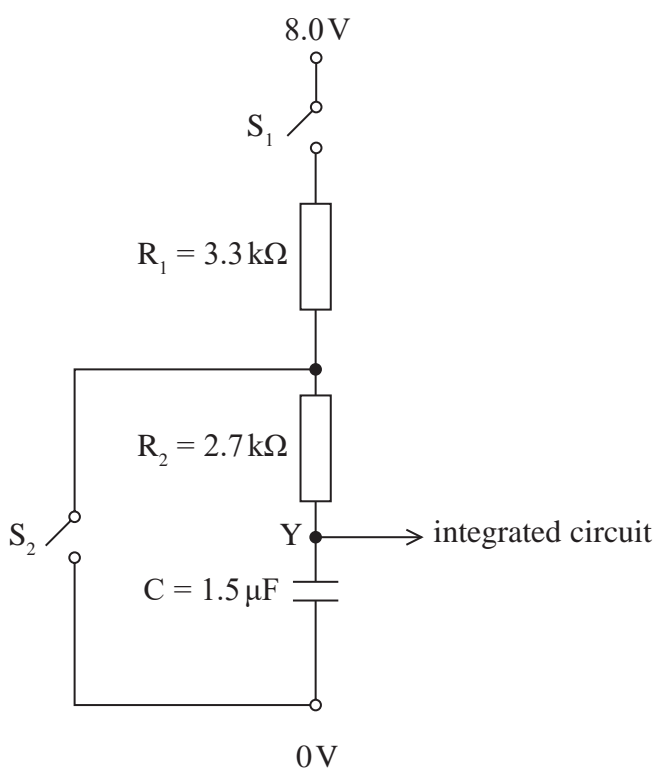


**15** The properties of capacitors make them useful in timing circuits.


The following circuit is used to provide an input Y to an integrated circuit.



(a) Initially the capacitor is uncharged. The switch  $S_1$  is closed.

Sketch a graph to show how the potential at point Y varies with time.

(3)

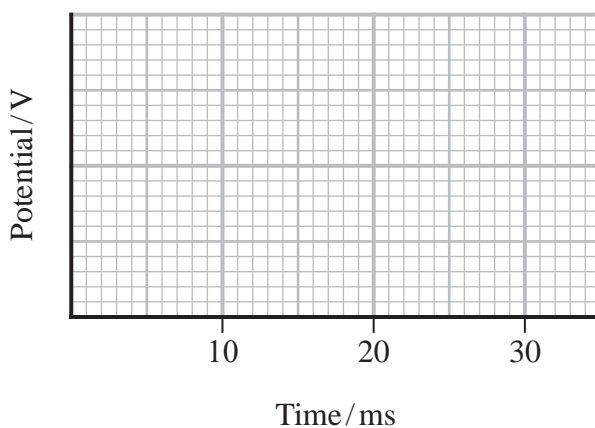

(b) When the potential at Y is 8.0 V, the switch  $S_2$  is closed.

(i) Calculate the time taken for the potential at Y to decrease to 2.0 V.

(3)

Time taken = .....

(ii) Calculate the energy stored on the capacitor when the potential at Y is 2.0 V.

(2)

Energy stored = .....

(c) When the potential at Y is 2.0 V, the switch  $S_2$  is opened.

Calculate the power dissipated by the resistance  $R_1$  when the potential at Y is 2.0 V.

(3)

Power dissipated = .....

(Total for Question 15 = 11 marks)