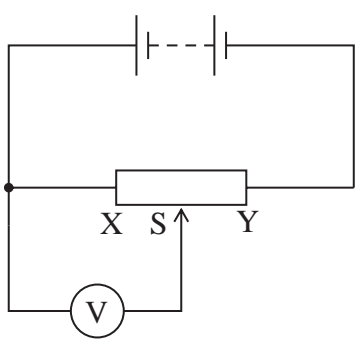


11 A student connected a voltmeter to a potential divider, as shown in the circuit diagram.




- (a) The potential divider was adjusted by moving sliding contact S from position X to position Y .

Explain how the voltmeter reading V depends upon the position of S .

(3)

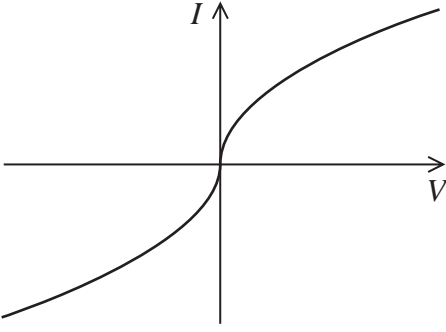- (b) A filament bulb and ammeter were connected to the potential divider. The potential divider was used to vary V across the filament bulb. The ammeter gave the corresponding current I in the filament.

I varied with V , as shown in the graph below.



Explain the shape of the graph.

(2)

- (c) The temperature T of the filament varies with the potential difference V across the filament according to the expression

$$T = aV^b$$

where a and b are constants.

- (i) Explain why a graph of $\log T$ against $\log V$ would give a straight line.

(2)

- (ii) Data for T and V is shown in the table below.

T / K	V / V		
1480	5.03		
1680	6.89		
1850	8.95		
2010	11.11		
2140	12.94		
2280	15.06		

Plot a graph of $\log T$ against $\log V$ on the grid opposite. Use the extra columns provided to show any processed data.

(5)

- (iii) Determine a value for b using your graph.

(2)

