
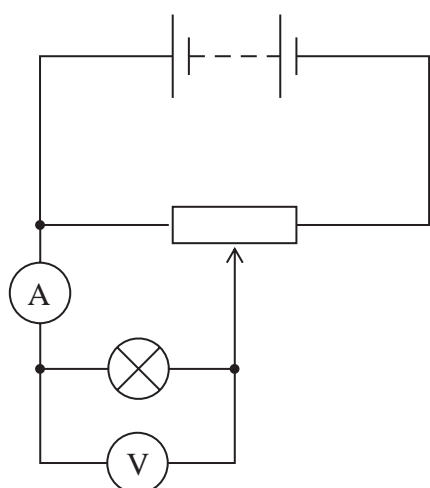


A student is planning to collect data to produce a current-potential difference graph for a filament lamp. Her teacher suggests two circuits that she could use.

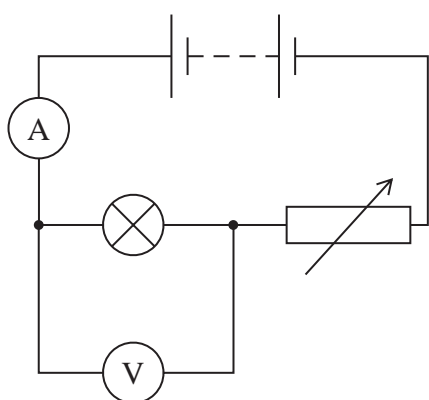

Circuit 1




Circuit 2

Circuit 1 uses a potential divider and circuit 2 uses a variable resistor to vary the potential difference across the filament lamp.

*(a) Discuss the suitability of each circuit to collect the data.

(6)

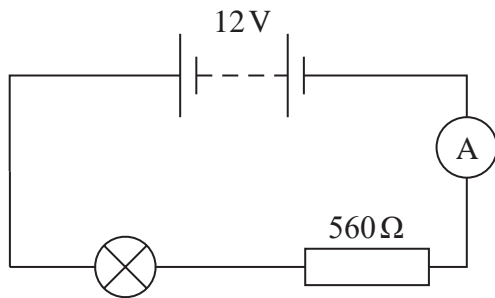(b) The student sets up the following circuit with the filament lamp. The battery has negligible internal resistance.




(i) The reading on the ammeter is 17.5 mA.

Calculate the value of the potential difference (p.d.) across the filament lamp.

(2)

p.d. across filament lamp =

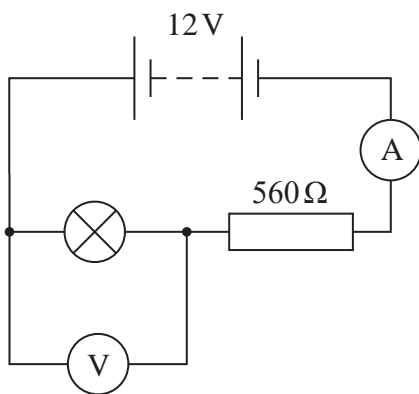(ii) When a voltmeter with a resistance of $1.5\text{ k}\Omega$ is connected as shown, the p.d. across the filament lamp decreases.



Explain why the p.d. across the filament lamp decreases.

(3)