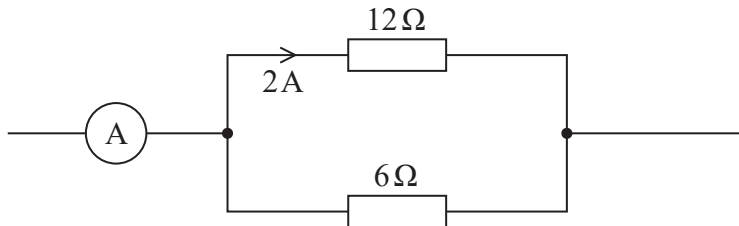


1 Part of an electric circuit is shown.



What is the current shown by the ammeter?

☐ A 3 A

☐ B 4 A

☐ C 5 A

☐ D 6 A

(Total for Question 1 = 1 mark)