

**5** Which of the following is the total resistance of the resistors in parallel?

☐ **A**  $20\ \Omega$

☐ **B**  $40\ \Omega$

☐ **C**  $90\ \Omega$

☐ **D**  $180\ \Omega$

**(Total for Question 5 = 1 mark)**