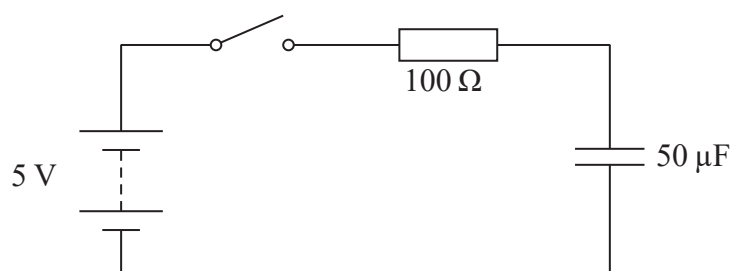



**15** A circuit consists of a battery of e.m.f. 5 V and negligible internal resistance, a switch, a 100  $\Omega$  resistor and an uncharged 50  $\mu\text{F}$  capacitor.




- (a) Describe what happens to the potential difference across the resistor and the potential difference across the capacitor after the switch is closed.

(4)

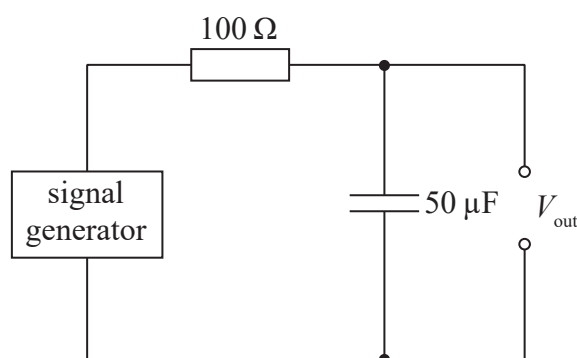- (b) The battery and switch are replaced by a signal generator providing a square wave output of peak potential difference 5 V. The signal generator has negligible internal resistance.



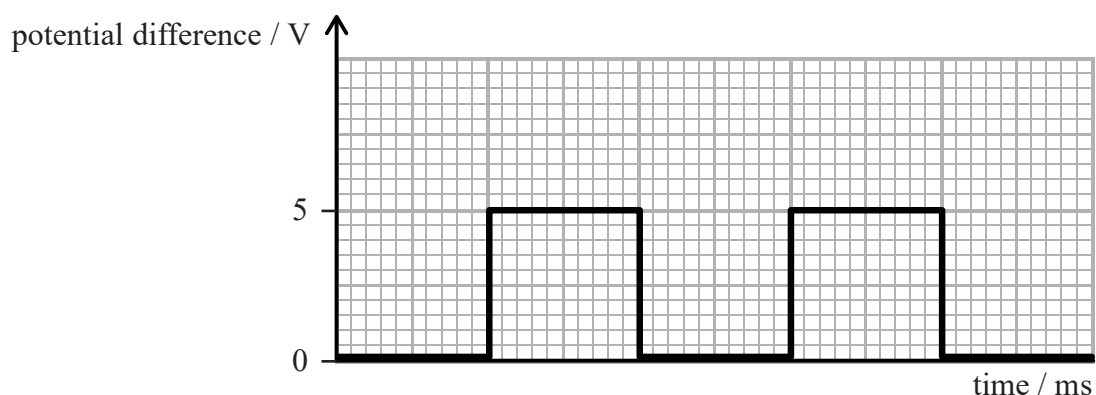The graph shows the square wave output of the signal generator. The frequency of the square wave is 20 Hz.



On the graph add values to the time axis and sketch a graph of the potential difference,  $V_{\text{out}}$ , across the capacitor for two cycles of the square wave. Assume the capacitor is initially uncharged.

(5)