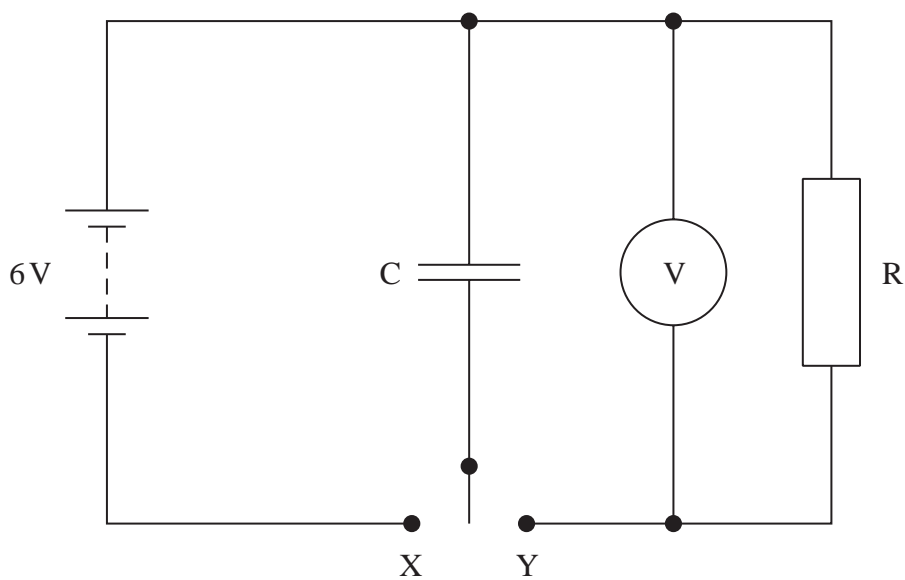



A student investigated the discharge of a capacitor C through a resistor R using the circuit shown.



The student used the switch to connect C to X to charge the capacitor. She then connected C to Y to discharge the capacitor through R .

As the capacitor discharged, she recorded values of the potential difference V across C and corresponding values of time t . She used a stopwatch to measure t .

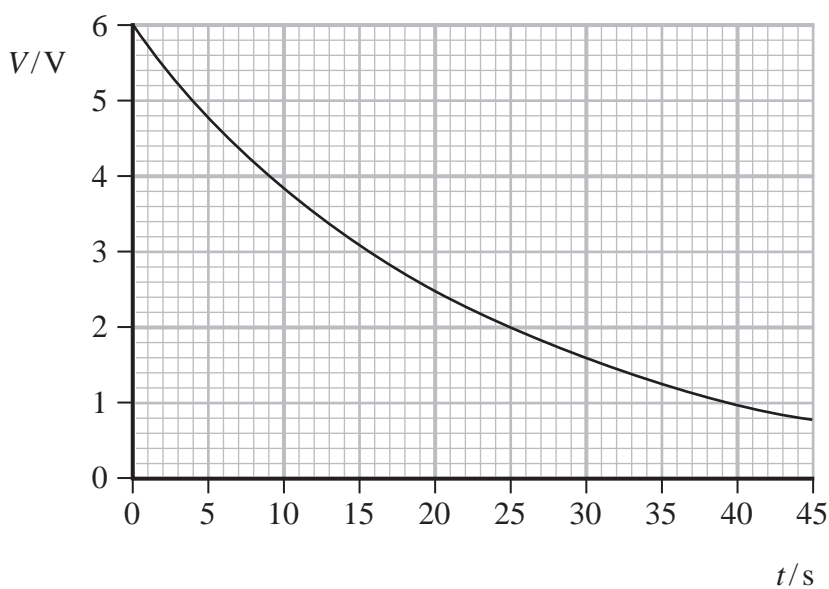The student used her results to plot the following graph.



- (a) The capacitor was marked $220\mu\text{F} \pm 20\%$.

Deduce whether the student's data give a value of capacitance within the stated range.

$$R = 82\text{ k}\Omega$$

(5)

- (b) The student suggested that her results would have been more accurate if she had used a data logger to record the data.

Assess the student's suggestion.

(3)