

4 Which of the following is the current I in ampere?

☐ **A** 3.0

☐ **B** 4.0

☐ **C** 5.0

☐ **D** 6.0

(Total for Question 4 = 1 mark)